



Vidyavardhini's College of Engineering and Technology

Department of Artificial Intelligence & Data Science

Experiment No. 3
To realize half adder and full adder.
Name: Nitish Jha
Roll Number: 18
Date of Performance:
Date of Submission:

Aim - To realize half adder and full adder.

Objective -

- 1) The objective of this experiment is to understand the function of Half-adder, Full-adder, Half-subtractor and Full-subtractor.
- 2) Understand how to implement Adder and Subtractor using logic gates.

Components required -

1. IC's - 7486(X-OR), 7432(OR), 7408(AND), 7404 (NOT)
2. Bread Board
3. Connecting wires.

Theory -

Half adder is a combinational logic circuit with two inputs and two outputs. The half adder circuit is designed to add two single bit binary numbers A and B. It is the basic building block for addition of two single bit numbers. This circuit has two outputs CARRY and SUM.

$$\text{Sum} = A \oplus B$$

$$\text{Carry} = A B$$

Full adder is a combinational logic circuit with three inputs and two outputs. Full adder is developed to overcome the drawback of HALF ADDER circuit. It can add two one bit numbers A and B. The full adder has three inputs A, B, and CARRY in, the circuit has two outputs CARRY out and SUM.

$$\text{Sum} = (A \oplus B) \oplus \text{Cin}$$

$$\text{Carry} = AB + \text{Cin} (A \oplus B)$$

Subtracting a single-bit binary value B from another A (i.e. A - B) produces a difference



Vidyavardhini's College of Engineering and Technology

Department of Artificial Intelligence & Data Science

bit D and a borrow out bit B-out. This operation is called half subtraction and the circuit to realize it is called a half subtractor. The Boolean functions describing the half- Subtractor are

$$\text{Sum} = A \oplus B$$


$$\text{Carry} = A' B$$

Subtracting two single-bit binary values, B, Cin from a single-bit value A produces a difference bit D and a borrow out Br bit. This is called full subtraction. The Boolean functions describing the full-subtractor are

$$\text{Difference} = (A \oplus B) \oplus \text{Cin}$$


$$\text{Borrow} = A'B + A'(\text{Cin}) + B(\text{Cin})$$

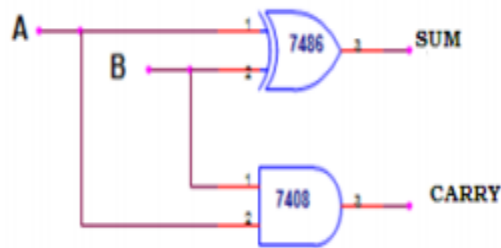Circuit Diagram and Truth Table - Half-adder



A	B	SUM	CARRY
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Full-adder

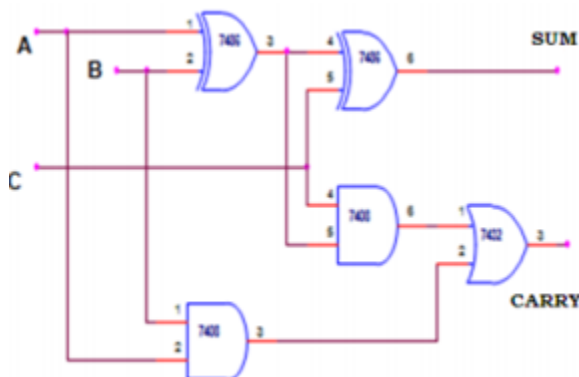

A	B	C	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1




Vidyavardhini's College of Engineering and Technology

Department of Artificial Intelligence & Data Science

Procedure -

1. Verify the gates.
2. Make the connections as per the circuit diagram.
3. Switch on VCC and apply various combinations of input according to truth table.
4. Note down the output readings for half/full adder and half/full subtractor, Sum/difference and the carry/borrow bit for different combinations of inputs verify their truth tables.

Output:-

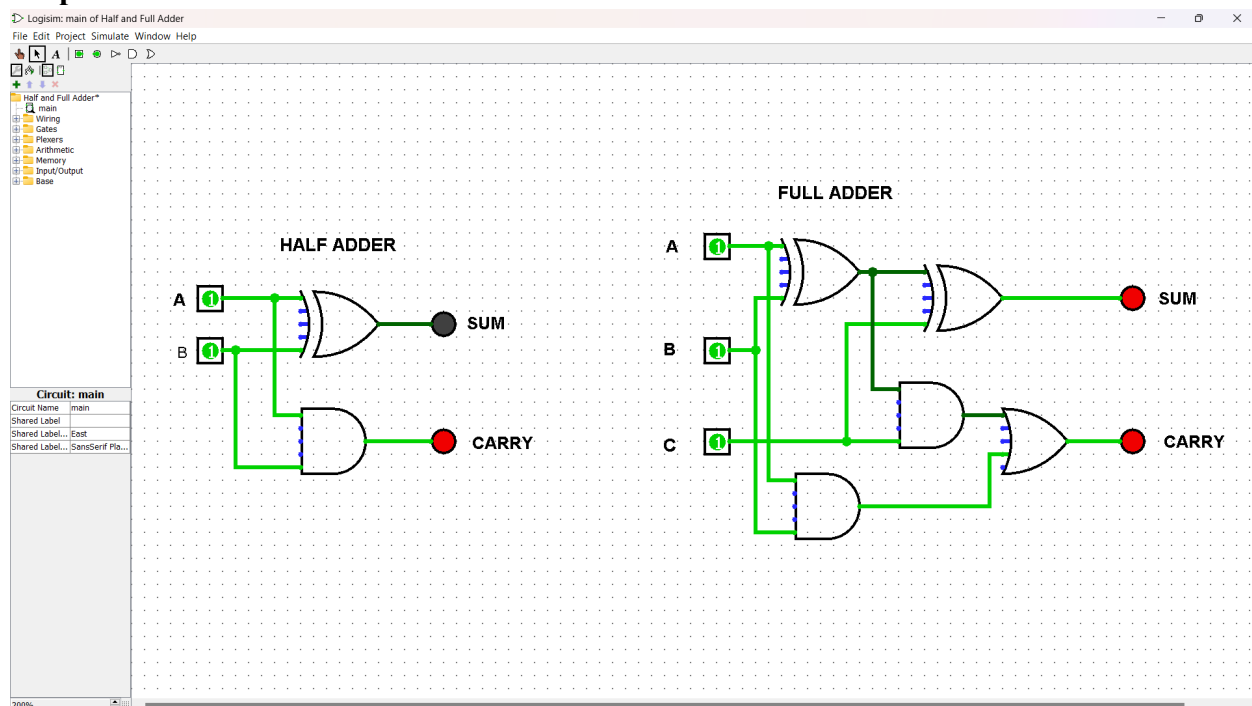



Vidyavardhini's College of Engineering and Technology

Department of Artificial Intelligence & Data Science

Conclusion -

A half adder is a digital circuit that can add two binary numbers and provide two outputs: the sum and the carry. However, it cannot account for a carry from a previous addition.

A full adder, on the other hand, is a more complex circuit that can add three binary numbers: A, B, and a carry from a previous addition. It produces two outputs: the sum and a carry-out. It is more versatile for multi-digit binary addition.